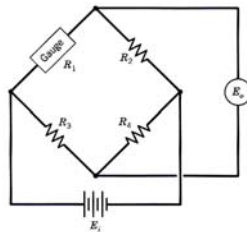


SE104 Homework 5

1. List three major reasons that may lead to failure of strain-gauge measurement.
2. A Wheatstone bridge is shown below. R_1 , R_2 , R_3 , and R_4 are four strain gauges having the same initial resistance of $120\ \Omega$. Their gauge factors are 2, 2, 10, 5, respectively. They are mounted on a rod. The Young's modulus of the rod material is 200 GPa and the Poisson's ratio is 0.3. The rod diameter is 10 cm and its length is 1 m. The rod is subjected to a tensile force. Gauges 1 and 4 are mounted along the axial direction, i.e. the loading direction. Gauges 2 and 3 are mounted along the transverse direction. The applied DC voltage on the bridge $E_i = 10\ \text{V}$. The bridge output $\delta E_o = 40\ \text{mV}$. (a) Is the bridge initially balanced? (b) What is the engineering strain along the loading direction? (c) What is the true strain? (d) What is the tensile force?



Hint: If $R_1 = R_2 = R_3 = R_4$, then

$$\frac{\delta E_o}{E_i} = \frac{1}{4}(\varepsilon_1 GF_1 - \varepsilon_2 GF_2 + \varepsilon_4 GF_4 - \varepsilon_3 GF_3)$$

It is possible to purchase matched sets of strain gauges for a particular application, so that $GF_1 = GF_2 = GF_3 = GF_4$, and

$$\frac{\delta E_o}{E_i} = \frac{GF}{4}(\varepsilon_1 - \varepsilon_2 + \varepsilon_4 - \varepsilon_3)$$

3. We have 4 identical strain gauges of the same initial resistance (R) and the same gauge factor (GF). They will be used as R_1 , R_2 , R_3 , and R_4 in a Wheatstone bridge, respectively. We want to measure the tensile strain of a rod subjected to a tensile force. What is the maximum bridge constant (κ) that we can reach? Clear state your assumptions.
4. Describe at least one method to eliminate the temperature effect in strain-gauge measurement.